
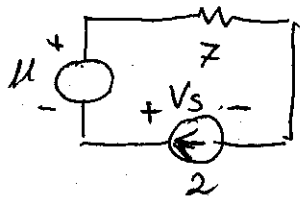


Nodo (A): $I_1 + 10 - 20 - 25 = 0 \Rightarrow I_1 = 35 \text{ A.}$

Nodo (B): $-15 + 20 + 25 - I_3 = 0 \Rightarrow I_3 = 30 \text{ A.}$

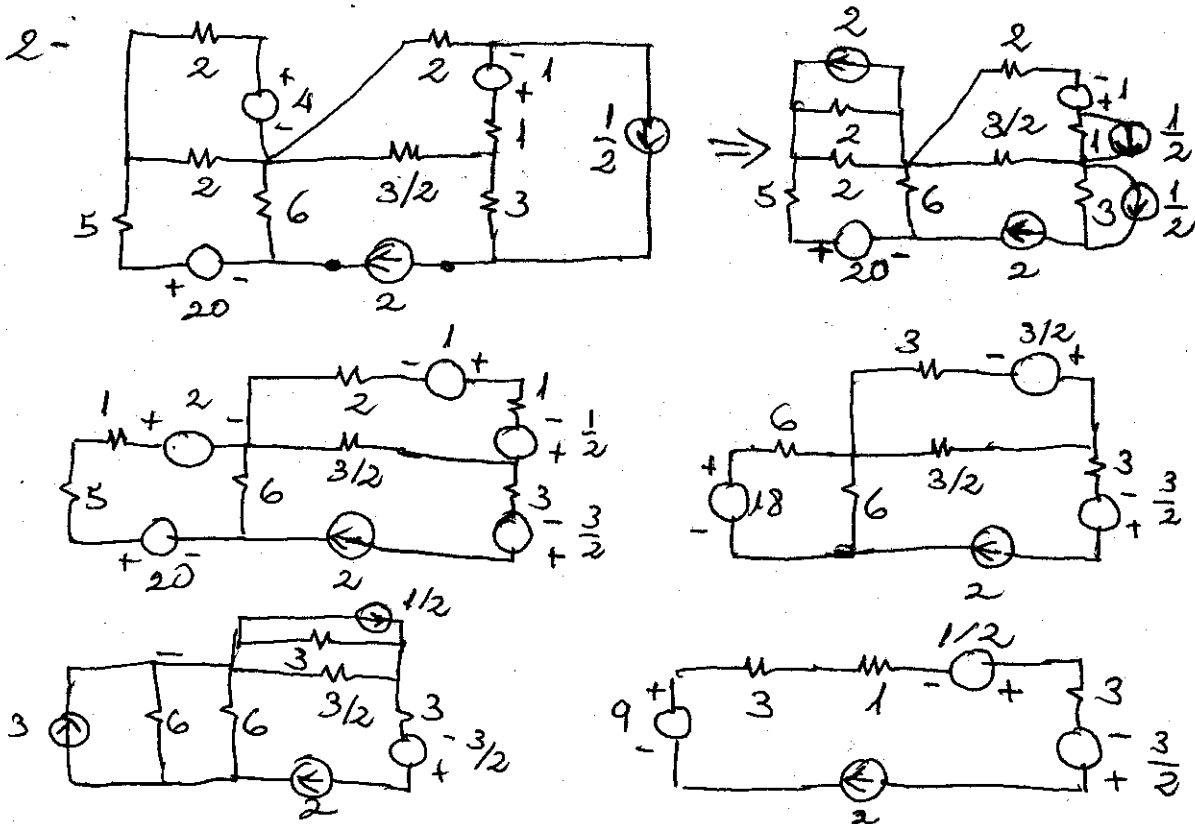Nodo (C): $-I_1 + I_2 + I_3 = 0 \Rightarrow I_2 = 5 \text{ A.}$



$$-11 + 2 \times 7 - V_s = 0$$

$$V_s = 3 \text{ V.} \Rightarrow P_s = -(3 \times 2) = -6 \text{ W}$$

LA FUENTE DE 2 A. ENTREGA 6 W.