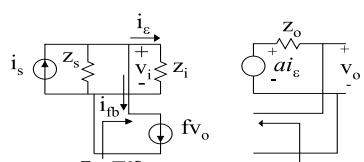
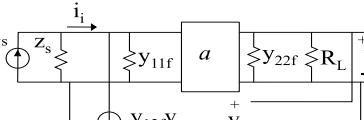
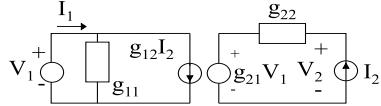
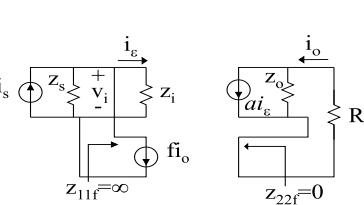
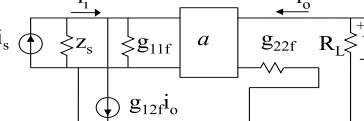
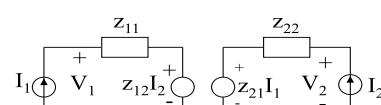
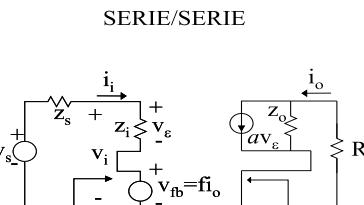
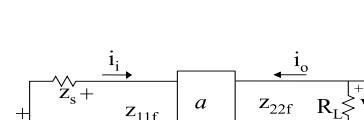
 <p>$I_1 = y_{11}V_1 + y_{12}V_2$ $I_2 = y_{21}V_1 + y_{22}V_2$</p> $y_{11} = \frac{I_1}{V_1} \Big _{V_2=0} \quad y_{12} = \frac{I_1}{V_2} \Big _{V_1=0}$ $y_{21} = \frac{I_2}{V_1} \Big _{V_2=0} \quad y_{22} = \frac{I_2}{V_2} \Big _{V_1=0}$	<p>PARALELO/PARALELO</p>  $A = \frac{v_o}{i_s} = \frac{a}{1+af} \quad Z_i = \frac{v_i}{i_i} = \frac{z_i}{1+af}$ $a = \frac{v_o}{i_s} \Big _{f=0} \quad Z_o = \frac{z_o}{1+af}$	 <p>$y_{12f} >> y_{12a}$ $y_{21f} << y_{21a}$</p> <p>Buen Amplificador de trans-resistencia $Z_i \downarrow \quad Z_o \downarrow$</p>
 <p>$I_1 = g_{11}V_1 + g_{12}I_2$ $V_2 = g_{21}V_1 + g_{22}I_2$</p> $g_{11} = \frac{I_1}{V_1} \Big _{I_2=0} \quad g_{12} = \frac{I_1}{I_2} \Big _{V_1=0}$ $g_{21} = \frac{V_2}{V_1} \Big _{I_2=0} \quad g_{22} = \frac{V_2}{I_2} \Big _{V_1=0}$	<p>PARALELO/SERIE</p>  $A = \frac{i_o}{i_s} = \frac{a}{1+af} \quad Z_i = \frac{v_i}{i_i} = \frac{z_i}{1+af}$ $Z_o = z_o(1+af)$	 <p>$g_{12f} >> g_{12a}$ $g_{21f} << g_{21a}$</p> <p>Buen Amplificador de trans-resistencia $Z_i \downarrow \quad Z_o \uparrow$</p>
 <p>$V_1 = z_{11}I_1 + z_{12}I_2$ $V_2 = z_{21}I_1 + z_{22}I_2$</p> $z_{11} = \frac{V_1}{I_1} \Big _{I_2=0} \quad z_{12} = \frac{V_1}{I_2} \Big _{I_1=0}$ $z_{21} = \frac{V_2}{I_1} \Big _{I_2=0} \quad z_{22} = \frac{V_2}{I_2} \Big _{I_1=0}$	<p>SERIE/SERIE</p>  $A = \frac{i_o}{v_s} = \frac{a}{1+af} \quad Z_i = \frac{v_i}{i_i} = z_i(1+af)$ $Z_L \ll z_o \quad Z_o = z_o(1+af)$	 <p>$z_{12f} >> z_{12a}$ $z_{21f} << z_{21a}$</p> <p>Buen Amplificador de trans-resistencia $Z_i \uparrow \quad Z_o \uparrow$</p>