


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

SERIE/PARALELO

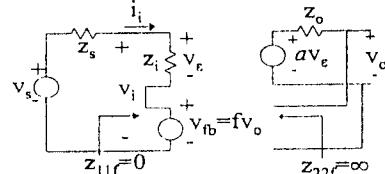


$$A = \frac{v_o}{v_s} = \frac{a}{1+af} \quad Z_i = \frac{v_s}{i_s} = z_i(1+af)$$

$$I_i = \frac{v_s}{z_i} \frac{1}{1+af} \quad Z_o = \frac{z_o}{1+af}$$

$|h_{12f}| >> |h_{12a}|$
 $|h_{21f}| << |h_{21a}|$

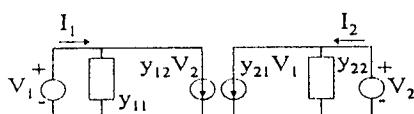Buen Amplificador de voltaje $Z_i \uparrow \quad Z_o \downarrow$




$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

PARALELO/PARALELO

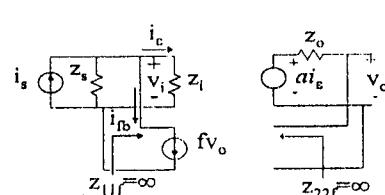


$$A = \frac{v_o}{i_s} = \frac{a}{1+af} \quad Z_i = \frac{v_s}{i_s} = \frac{z_i}{1+af}$$

$$\alpha = \frac{v_o}{i_s} \Big|_{f=0} \quad Z_o = \frac{z_o}{1+af}$$

$|y_{12f}| >> |y_{12a}|$
 $|y_{21f}| << |y_{21a}|$

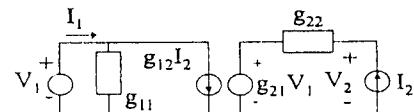Buen Amplificador de trans-resistencia $Z_i \downarrow \quad Z_o \downarrow$




$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

PARALELO/SERIE

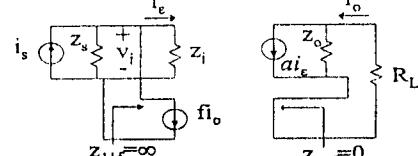


$$A = \frac{i_o}{i_s} = \frac{a}{1+af} \quad Z_i = \frac{v_s}{i_s} = \frac{z_i}{1+af}$$

$$Z_o = z_o(1+af)$$

$|g_{12f}| >> |g_{12a}|$
 $|g_{21f}| << |g_{21a}|$

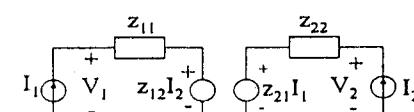Buen Amplificador de trans-resistencia $Z_i \downarrow \quad Z_o \uparrow$




$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

SERIE/SERIE

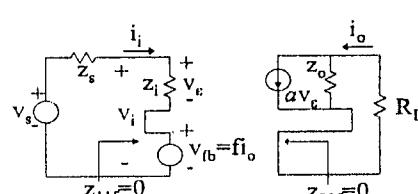

$$A = \frac{i_o}{v_s} = \frac{a}{1+af} \quad Z_i = \frac{v_s}{i_s} = z_i(1+af)$$

$$Z_o = z_o(1+af)$$

$|z_{12f}| >> |z_{12a}|$
 $|z_{21f}| << |z_{21a}|$

Buen Amplificador de trans-resistencia $Z_i \uparrow \quad Z_o \uparrow$